

CSE 260M / ESE 260
Intro. To Digital Logic & Computer Design

Bill Siever
&
Jim Feher

This week

- Office hours posted! <https://wustl-cse260m-fl24.github.io/>
- Hw#2 Clarification

Review

- K-Maps: What & why?


K-Maps

Goal: Store Data

Stable, Reinforcing Setup: SR Latch

- On-line Demo: <https://logic.ly/>
 - Bistable: Two stable configurations
- Goal: Met!
 - S=Set, R=Reset

SR Latch

 


Goal: Store Data

- Set/Reset is *inconvenient*
 - We want something like, $\text{data} = X$, where x is 0 or 1 (store X , not “set or reset data based on X ”)
 - We want to store X in data *when we're ready to!*
- *Clock (Clk)*: Indicates *when* we want to change the data

D-Latch

- Start with SR Latch

 


- Describe Desired Behavior (of output, Q)

CLOCK	DATA	Q
0	0	(Unchanged)
0	1	(Unchanged)
1	0	0
1	1	1

D-Latch

- Start with SR Latch

 


- Describe Desired Behavior (of output, Q)

CLOCK	DATA	Q
0	0	
0	1	
1	0	0
1	1	1

D-Latch

- Start with SR Latch

 


- Describe Desired Behavior (of output, Q)

CLOCK	DATA	Q
0	0	
0	1	
1	0	RESET
1	1	SET

D-Latch

- Start with SR Latch

 


- Describe Desired Behavior (of output, Q)
- Just combinational logic

CLOCK	DATA	Q
0	0	
0	1	
1	0	RESET
1	1	SET

D-Latch

- Start with SR Latch

 


- Describe Desired Behavior (of output, Q)
- Just combinational logic
- Reset = Clock * /Data
Set = Clock * Data

CLOCK	DATA	Q
0	0	
0	1	
1	0	RESET
1	1	SET

Updates: <https://logic.ly/>

D-Latch

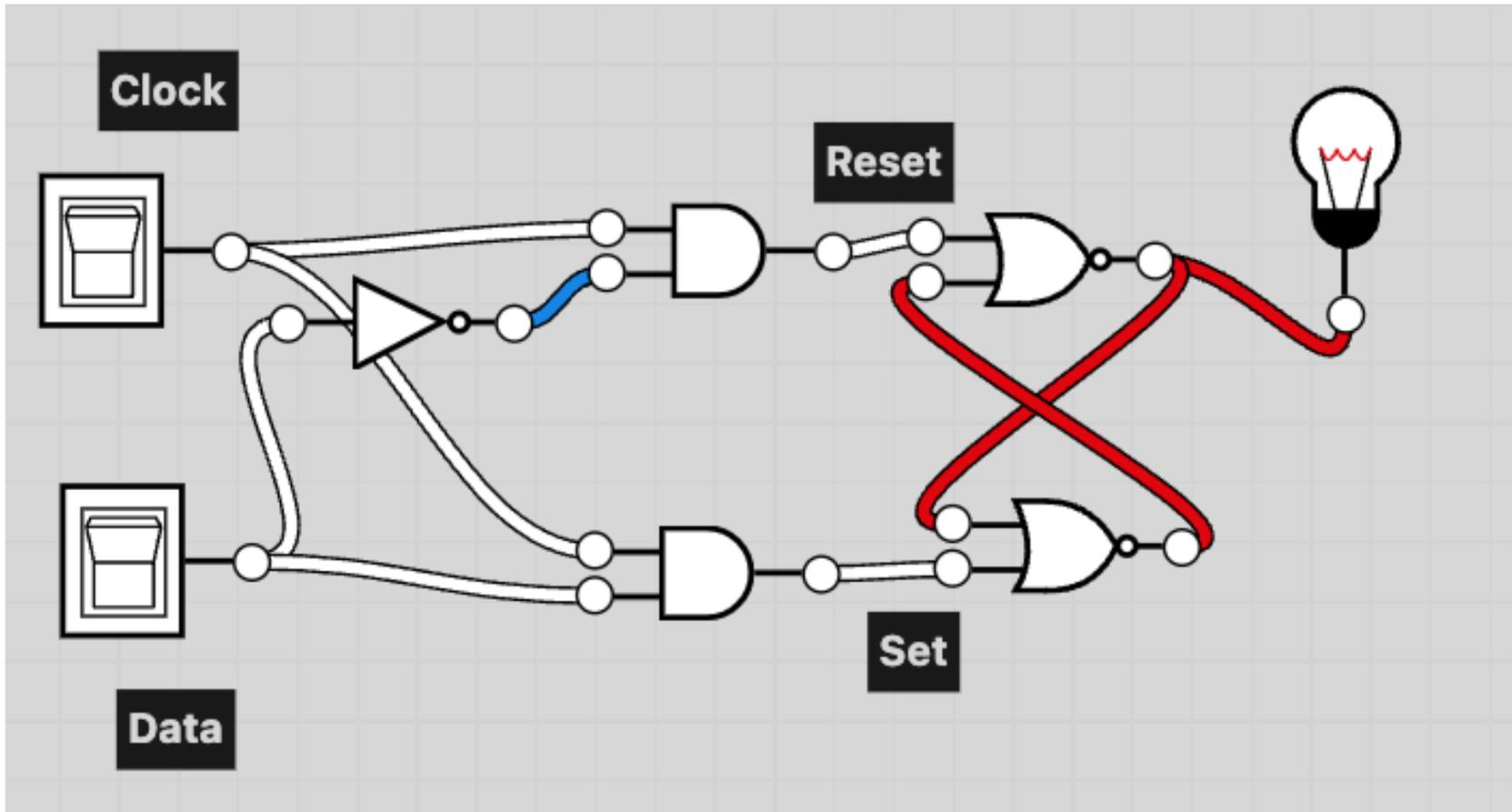


D-Latch

- “Latches on” to last data value when clock goes low
- Is sensitive to the *level* of the clock
- Is “transparent” when the clock is high

Goal: Store Data

- D-Latch is still a bit *inconvenient*
 - We'd like something like a (simple) camera
 - Instant shutter is “pressed” we capture data

Flip-Flop

 


<https://openclipart.org/detail/288726/flip-flops-4>

D Flip-Flop

- Two D-Latches with clocks in opposite states (via an inverter)
 - First stage: Transparent when clock is Low
 - Second stage: Transparent when clock is High
 - Effect: Capture D at precise instant clock goes from low to high
 - I.e. the clock EDGE
 - Edge triggered. Specifically, Rising Edge Triggered


Signal Edges

 

https://www.ni.com/docs/en-US/bundle/ni-hsdio/page/hsdio/fedge_trigger.html

“Enable”

 - We may want to have two things control timing: the clock and an enable
- Ex: $X[0] = 1$ (in a program) . We only want to modify X *when that line runs*.



Combinational Logic

- (Purely) combines current inputs to produce output
 - Doesn't depend on past inputs
 - Can be represented with a simple table
 - One-way: Doesn't have any feedback paths from output back to inputs



Sequential & Synchronous Logic

- Need to know sequence of inputs
- Can't be represented with a *simple* table of just inputs and outputs
(Possibly a complex table of history of inputs and outputs)

Synchronous Sequential Circuits

- *Are synchronized* by a common clock
- Uses registers
- Mix of registers and combinational logic
- Cycles include at least one register
- Goal: Impose predictable behavior!

Finite State Machines

- State: A condition of being
- Finite: Er. Finite
 - Real machine has real-world limitations: $k \times$ D-latches
 - k D-Latches means $\leq 2^k$ states (finite)

Questions

- [Favorite vacation spot?]
- [Exams: Like Hw?]: Yep.
- [State Machine Encoding Choices?]
Memory vs. Logic: They can impact complexity of combinational logic.
(Typically One-hot: more memory, but simpler logic)
- [FSMs? Mealy? Moore?]: More (Moore?) next time
- [I don't get/understand Latches/Edges/Levels/etc.]
- [Which memory things are important]: (Rising) Edge Triggered D-latch.
(Most others were just part of the journey to it)
- [Starbursts Dissolve in Hair Cream]? Whahhh????

Next Time

- Studio
- Homework 2 due Thursday night!